

Chapter 6 Dynamic Op Amp Limitations


- Unity-gain frequency, f_t
- Gain-bandwidth product, GBP
- Closed-loop bandwidth, f_A
- Full-power bandwidth, FPB
- Rise time, t_r
- Slew rate, SR
- Settling time, t_s
- Current-feedback amplifier (CFA) → very high speed applications
- Most op amps are internally compensated for stability: \Rightarrow dominant pole compensation

6.1 Open-Loop Response

$$a(jf) = \frac{a_0}{1 + jf/f_A} \quad ; \quad \text{dominant pole compensation}$$

$$\begin{cases} a_0 & : \text{open-loop dc gain} \\ f_A & : \text{open-loop } -3\text{dB freq. OR} \\ & \text{open-loop bandwidth} \end{cases}$$

$$|a(jf)| = \frac{a_0}{\sqrt{1 + (f/f_A)^2}}, \quad \angle a(jf) = -\tan^{-1} \frac{f}{f_A}$$

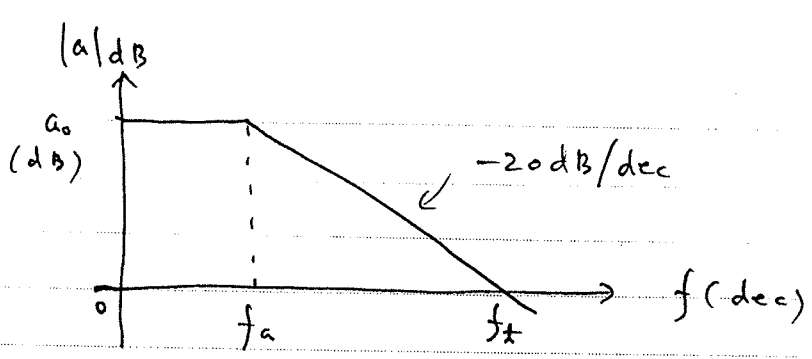

f_t : unity-gain freq. OR transition freq.

at $f = f_t$, $1 = a_0 / \sqrt{1 + (f_t/f_a)^2}$
 since $f_t \gg f_a$, $f_t = a_0 f_a$.

For 741, $a_0 = 200,000$, $f_a = 5 \Rightarrow f_t = 1 \text{ MHz}$

$$\left\{ \begin{array}{l} a(jf) |_{f \ll f_a} \rightarrow a_0 \angle 0^\circ \\ a(jf) |_{f = f_a} = \frac{a_0}{\sqrt{2}} \angle -45^\circ \\ a(jf) |_{f \gg f_a} \rightarrow \frac{f_t}{f} \angle -90^\circ \end{array} \right.$$

For $f \gg f_a$, $\text{GBP} = |a(jf)| \times f = f_t$


\Rightarrow Dominant pole compensation \Rightarrow constant-GBP op amp

$$|a(jf_0)| = \frac{f_t}{f_0} = a_0 \frac{f_a}{f_0}$$

- Most op amps : $\text{GBW} = 500 \text{ kHz} \sim 20 \text{ MHz}$
- f_t is a stable parameter
 (a & a_0 are not stable)

* Loop Gain, $T = a\beta = a/(1/\beta)$

$$\left\{ \begin{aligned} |T|_{dB} &= 20 \log_{10} |T| = 20 \log_{10} |a| - 20 \log_{10} \left| \frac{1}{\beta} \right| \\ &= |a|_{dB} - |1/\beta|_{dB} \\ \angle T &= \angle a - \angle \left(\frac{1}{\beta} \right) \end{aligned} \right. \quad \text{Fig. 6.3)$$

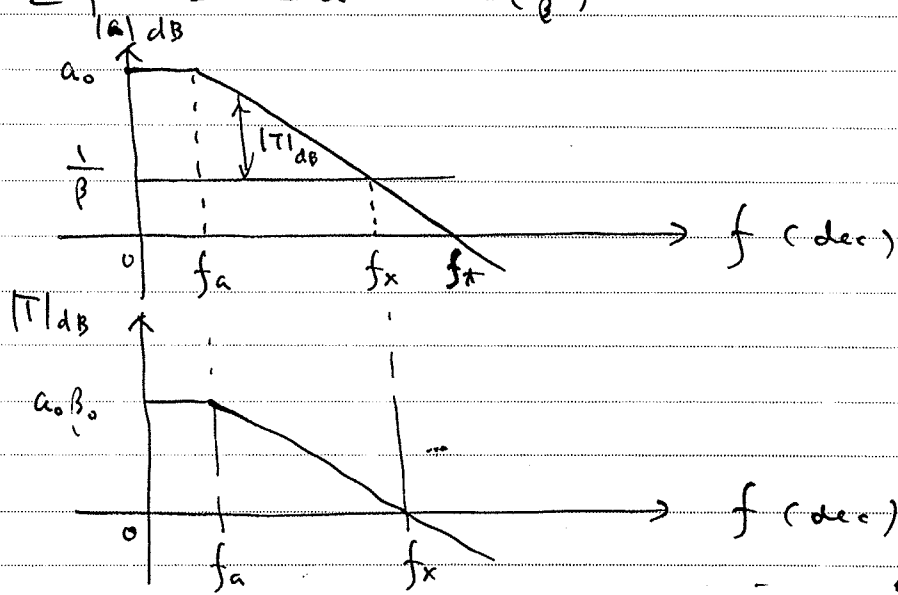

$f_x =$ crossover freq.

$$|T(jf_x)|_{dB} = 0 \quad \text{OR} \quad |T(jf_x)| = 1$$

For $f \ll f_x$, $|T| \gg 1 \Rightarrow$ negative feedback is effective. nearly ideal.



b.2 Closed-loop Response

$$A(jf) = A_{ideal} \cdot \frac{1}{1 + 1/T(jf)}$$

$$\epsilon_m = \left| \frac{1}{1 + 1/T(jf)} \right| - 1 \quad : \text{magnitude error}$$

$$\epsilon_\phi = - \angle [1 + 1/T(jf)] \quad : \text{phase error}$$

* Noninverting Amplifier

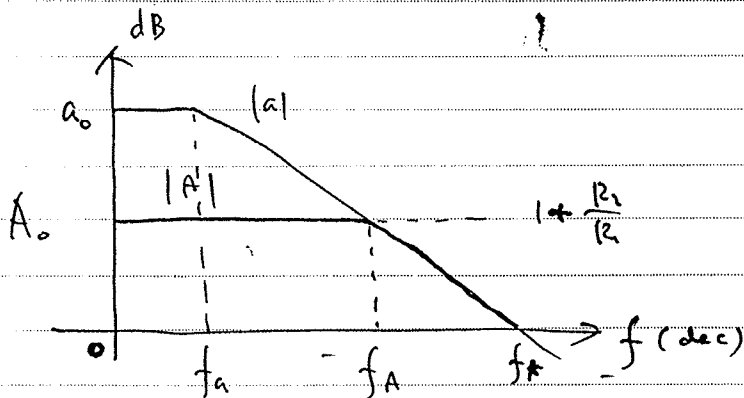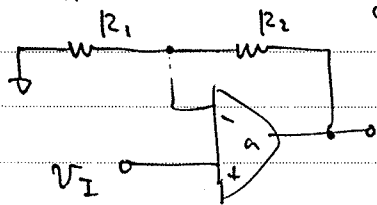

$$A(jf) = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{1 + \left(1 + \frac{R_2}{R_1}\right) (1 + jf/f_a) / a_0}$$

$$= \frac{A_0}{1 + jf/f_A}$$

where $A_0 = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{1 + \left(1 + \frac{R_2}{R_1}\right) / a_0}$

$$f_A = f_a \left(1 + a_0 \frac{R_1}{R_1 + R_2}\right)$$

for $a_o \gg 1 + R_2/R_1$,

$$A(jf) = A_o \frac{1}{1 + jf/f_A}$$

where $A_o \doteq 1 + \frac{R_2}{R_1}$, $f_A \doteq \beta f_x$

$$\beta = \frac{R_1}{R_1 + R_2} = \text{feedback factor}$$

$$f_x = a_o f_a = \text{unity-gain freq.}$$


$\Rightarrow \begin{cases} f_A : -3 \text{ dB freq. OR closed-loop bandwidth} \\ A_o : \text{closed-loop dc gain} \end{cases}$

② Example 6.1

* Gain-Bandwidth Tradeoff "figure of merit"

$$GBP = A_o f_A = f_x \quad \text{of an op amp}$$

② Example 6.2

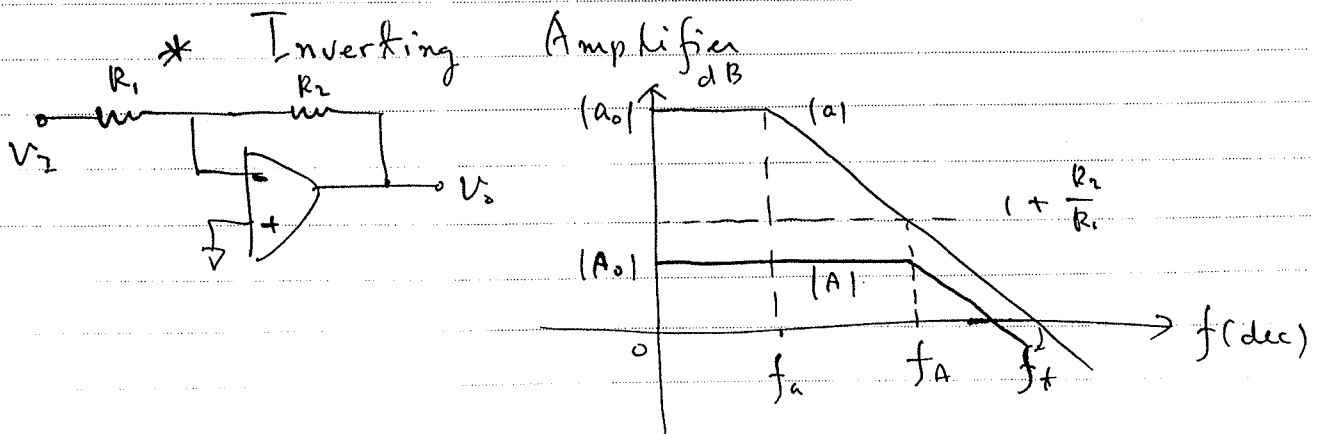

$$A(jf) = A_0 \frac{1}{1 + jf/f_A}$$


$$A_0 \approx -\frac{R_2}{R_1}, \quad f_A \approx \beta f_T$$

$$\beta = \frac{R_1}{R_1 + R_2}$$

} when $a_0 \gg 1 + \frac{R_2}{R_1}$

$$\begin{aligned} \text{GBP} &= |A_0| \cdot f_A = \frac{R_2}{R_1} \times f_T \frac{R_1}{R_1 + R_2} \\ &= \frac{R_2}{R_1 + R_2} f_T \end{aligned}$$

b.3 Input and Output Impedances

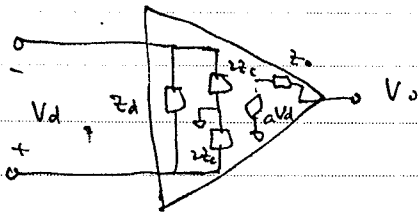

Z_d : differential input impedance
 Z_c : common-mode input impedance
 Z_o : output impedance



BJT : V_d & $V_c \sim \text{M}\Omega$ or $\text{G}\Omega$, $V_c \gg V_d$

FET : $V_d \doteq V_c \sim > 100 \text{ G}\Omega$

At high freq, $\left\{ \begin{array}{l} Z_d \text{ becomes } \text{capacitive} \\ Z_o \text{ " } \text{inductive} \end{array} \right.$

b.4 Transient Response

* Rise Time, t_R

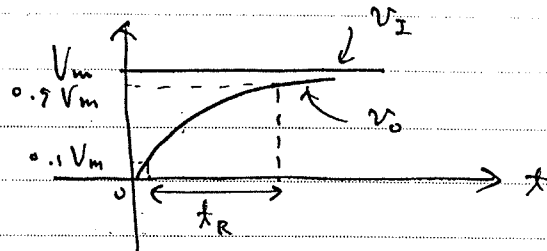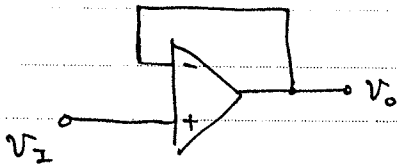

$$A(jf) = \frac{1}{1 + jf/f_x}$$

$$v_I(t) = V_m u(t) \Rightarrow v_o(t) = V_m (1 - e^{-t/\tau})$$

$$\tau = \frac{1}{2\pi f_x}$$

$$t_R = \tau (\ln 0.9 - \ln 0.1)$$

$$= \frac{0.35}{f_x}$$

Ex1. $f_x = 100 \text{ kHz} \Rightarrow t_R \approx 350 \text{ ns}$

* Slew - Rate

for the step response above,

$$\left. \frac{dv_o}{dt} \right|_{\max} = \left. \frac{dv_o}{dt} \right|_{t=0} = \frac{V_m}{\tau}$$

In order to get the same τ , we need $\frac{dv_o}{dt} \propto V_m$

However, $\frac{dv_o}{dt}$ saturates to a constant value called SR.

$$V_{om(crit)} = \frac{SR}{2\pi f}$$

↳ critical output-step magnitude at the onset of SR limiting.

* Full-power Bandwidth

For a sinusoidal input, $v_o(t) = V_{om} \sin 2\pi f t$.

$$\frac{dv_o(t)}{dt} = 2\pi f V_{om} \cos 2\pi f t \Rightarrow \left. \frac{dv_o}{dt} \right|_{\max} = 2\pi f V_{om}$$

Before SR limiting, $2\pi f V_{om} \leq SR$ OR

$$f V_{om} \leq \frac{SR}{2\pi}$$


↓

$$\left. \begin{array}{l} f \uparrow \text{ 이면 } V_{om} \approx \frac{SR}{2\pi} \\ V_{om} \uparrow \text{ 이면 } f \approx \frac{SR}{2\pi} \end{array} \right\} \text{ trade off}$$

$$FPB = \frac{SR}{2\pi V_{sat}} \quad : \quad \text{full-power bandwidth}$$

$f < FPB \Rightarrow v_o(t) \text{ 가 } \pm V_{sat} \text{ 이 아니라 SR limiting 이란 } \frac{SR}{2\pi} \text{ 이고.}$

* Settling Time, t_s

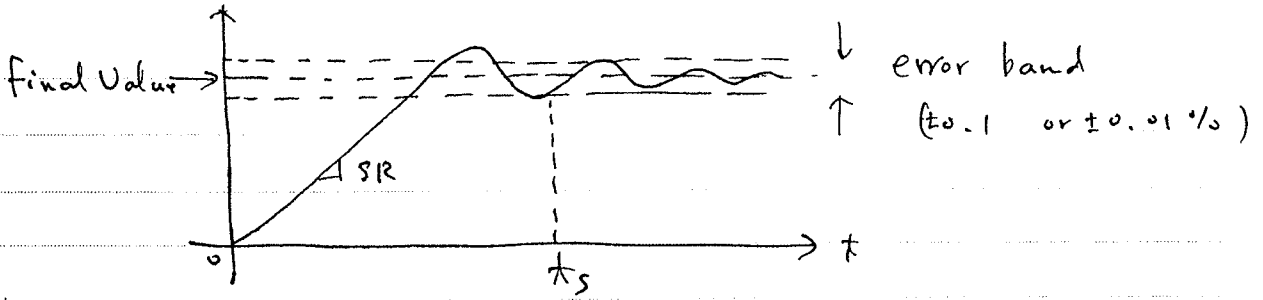

b.5

H/w : b.10 (c) ,