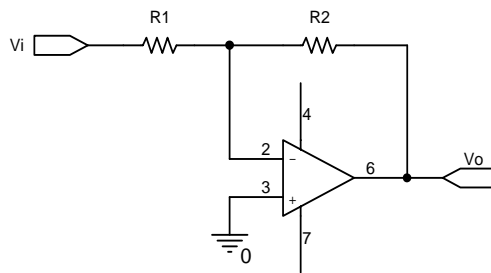


2003 1 II

* 20 , 가 .
 * 0 .

(1) , 100KΩ


$v_s(t) = 10 \sin(2\pi \times 10^{-3} t)$ mV 100 .



(a) 가 , R1 R2

(b) $v_s(t)$ $v_o(t)$, 0 ~ 2 ms .

(2) v_o v_1 v_2 .

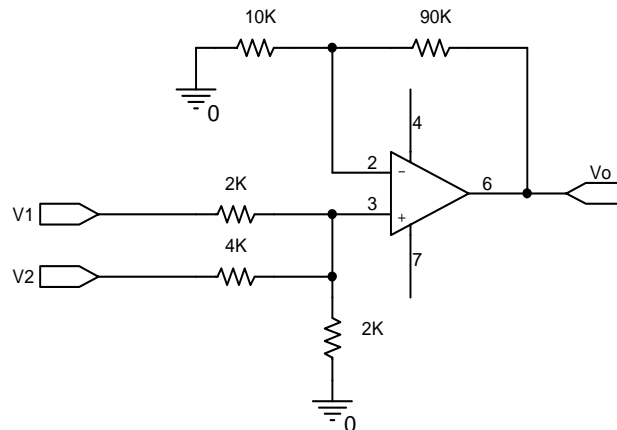

(3)

(a) v_o


v_1 v_2

(b)


OP amp

가 ,

R_x

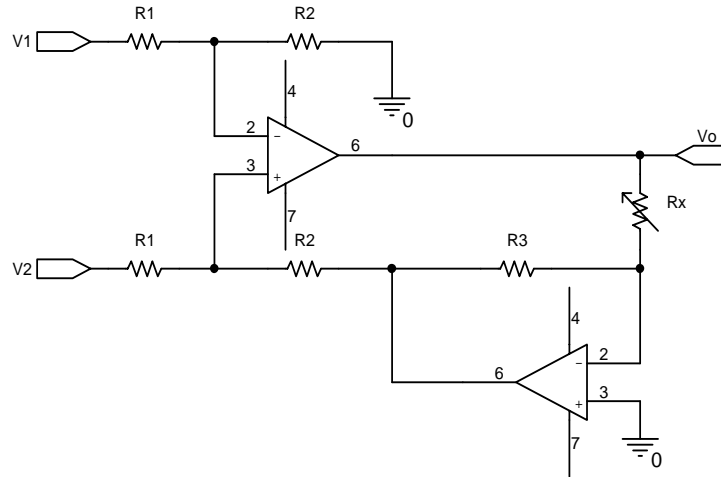

(4)

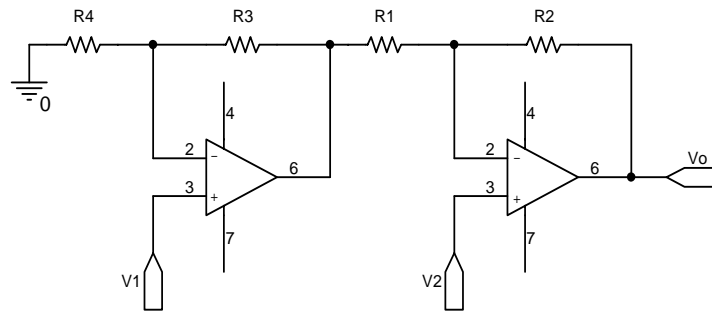


(a) $R_3/R_4 = (R_1/R_2)(1-\epsilon)$, $v_o = A_{dm}v_{DM} + A_{cm}v_{CM}$ A_{dm} A_{cm} ,

$CMRR$

(b) $R_2/R_1=100$, 0.5% , $CMRR$?

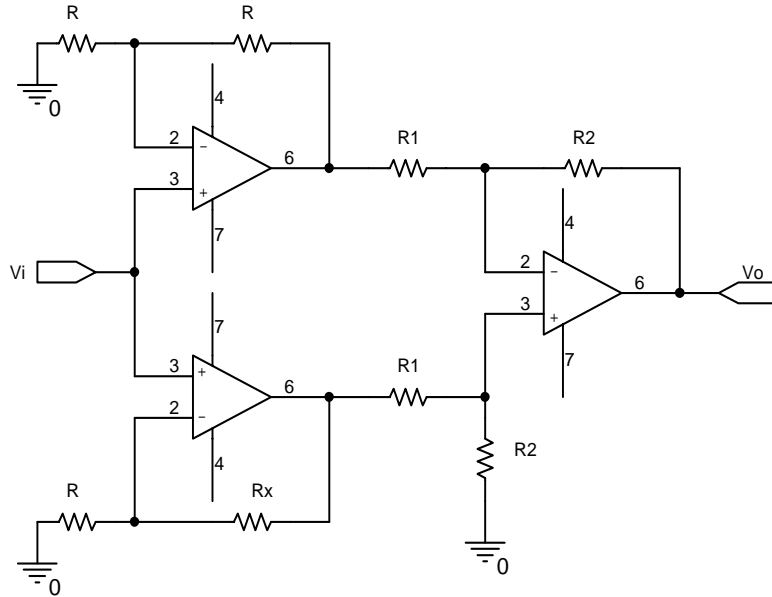- (5) R_x strain gage, $R_x = (1 + \delta)R$, δ strain gage strain $\epsilon = \frac{\Delta l}{l}$, $\delta = 2\epsilon$ 가 ., stress(σ) strain $\sigma = E\epsilon$, E Young's modulus .



- (a) v_o v_i , ϵ , R_1 , R_2 .
 (b) $v_i = 1$ V, 가 stress strain 가 ± 0.005 , $\pm 5V$ 가 R_1 R_2 .
 (c) 가 bridge 가 .
 (d) v_o 가 $0 \sim 10$ V 가, $\pm 15V$ dc 가 .