

2001년 1학기 계측회로 II

기말고사 해답

(1)

$$(a) \quad K = 1 + \frac{R_4}{R_3}$$

$$V_o = K \frac{1}{1 + sR_2C_2} V_i$$

$$\frac{V_i - V_i}{R_1} + \frac{V_o/K - V_i}{R_2} + \frac{V_o - V_i}{1/sC_1} = 0$$

$$\therefore H(s) = \frac{V_o}{V_i} = \frac{K}{R_1C_1R_2C_2s^2 + [(1-K)R_1C_1 + R_1C_2 + R_2C_2]s + 1}$$

$$(b) \quad \omega_o = \frac{1}{RC}, \quad \theta = \frac{1}{3-K}$$

$$RC = \frac{1}{2\pi f_o} = \frac{1}{2\pi \times 30} = 5.3 \times 10^{-3}$$

$$C = C_1 = C_2 = 0.1 \mu F$$


$$R = R_1 = R_2 = 53 k\Omega$$

$$K = 3 - \frac{1}{\theta} = 3 - \frac{1}{0.707} = 1.586 = 1 + \frac{R_4}{R_3}$$

$$R_3 = 10 k\Omega, \quad R_4 = 5.86 k\Omega$$



$$(c) \quad H_{oup} = K = 1.586$$

(2)

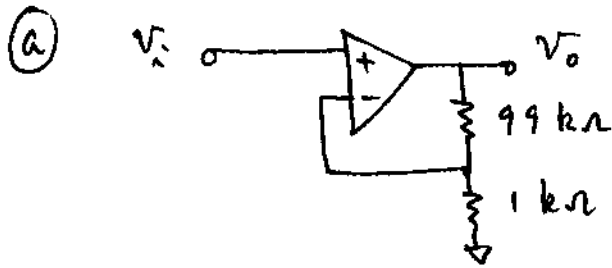

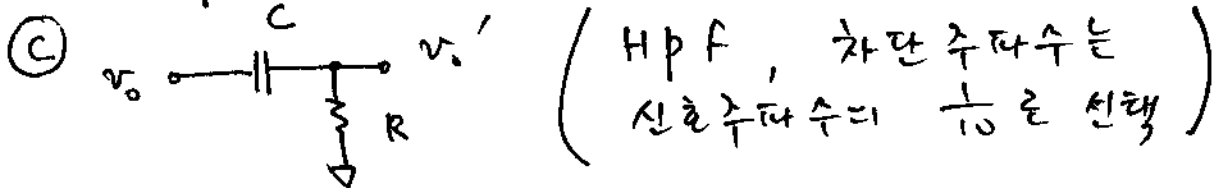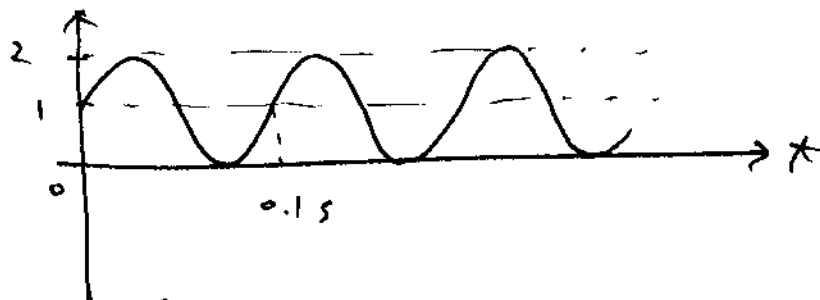(b) $v_i = 10 \sin(2\pi \times 100t) \text{ mV}$

$v_o = \sin(2\pi \times 100t) + 1 \text{ V}$



$$\frac{1}{2\pi R C} = 10, \quad R C = \frac{1}{2\pi \times 10} = 1.59 \times 10^{-2}$$

$$C = 0.1 \mu\text{F}, \quad R = 159 \text{ k}\Omega$$

(d) 위 HPF의 전달 함수 $H'(j\omega)$

$$H'(j\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega R C}{1 + j\omega R C}$$

신호 주파수 $f_s = 100 \text{ Hz}$ 에서


$$H'(j2\pi \times 100) = \frac{j9.9}{1 + j9.9} = 0.9949 / 5.77^\circ$$

신호 감쇠 = $20 \log 0.9949 = -0.044 \text{ dB}$

위상 지연 = 5.77°

(3)

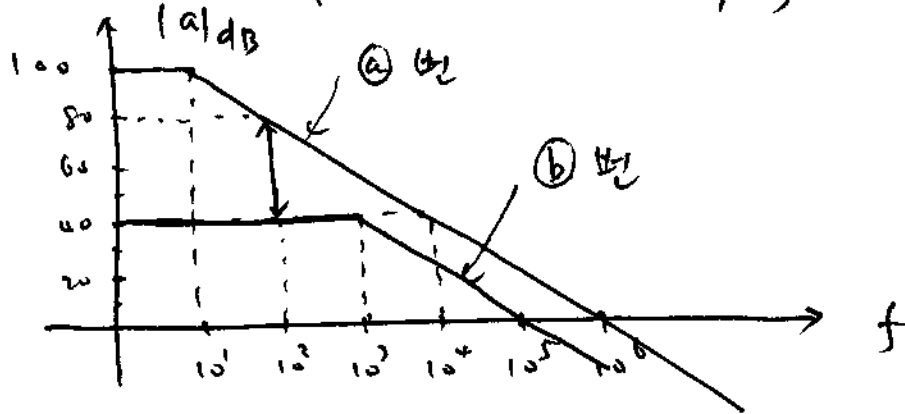
(a) $GBP = 10^6$, $a_0 = 100 \text{ dB}$, $f_a = 10 \text{ Hz}$



(b)

$A_v = 100 \cdot 1 \text{ V/V}$ $BW = \frac{10^6}{10^2} = 10^4 \text{ Hz}$

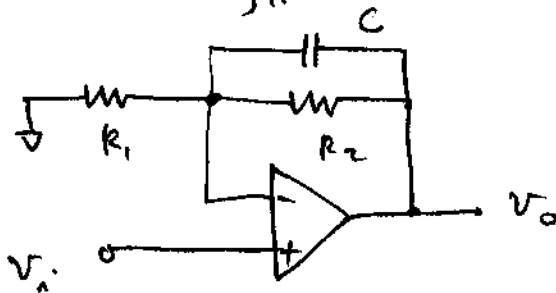따라서 $f_A = 10^3 \text{ Hz}$ 은 CH 의 제한이 될 것으로 보인다.



$R_1 = 1 \text{ k}\Omega$, $R_2 = 99 \text{ k}\Omega$

$\frac{1}{2\pi R_2 C} = 10^3 \text{ MHz}$ $C = 1.6 \text{ nF}$


$f = 100 \text{ Hz}$ MHz $\text{loop gain} = 40 \text{ dB}$

(c)

$A_v = 1000 \cdot 1 \text{ V/V}$



$f_A = \frac{10^6}{10^3} = 10^3 \text{ Hz}$

(4)

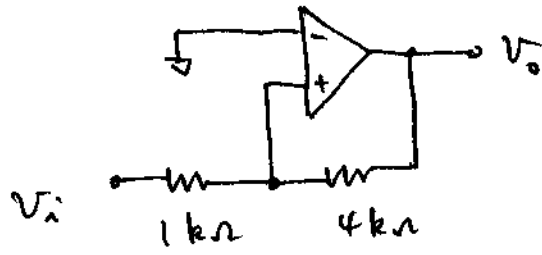


$$V_{sat} = \pm 10V$$

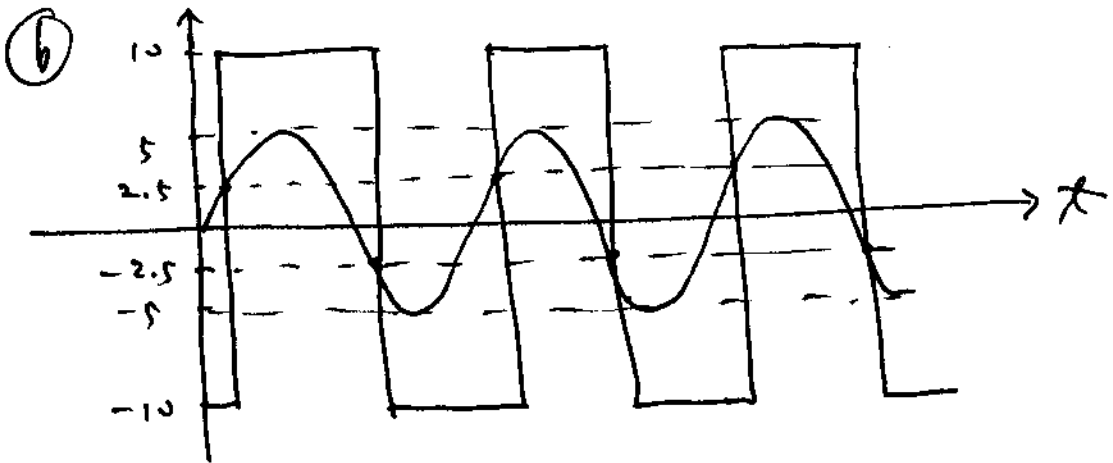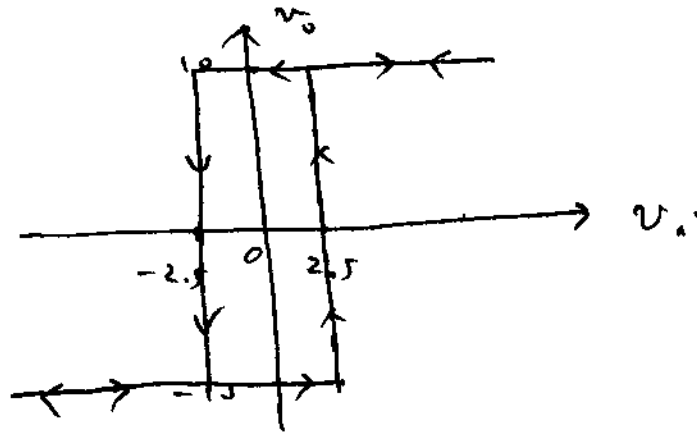(a) $V_{TH} = \frac{1}{4} \times 10 = 2.5V$
 $V_{TL} = -\frac{1}{4} \times 10 = -2.5V$



(5)

(a)

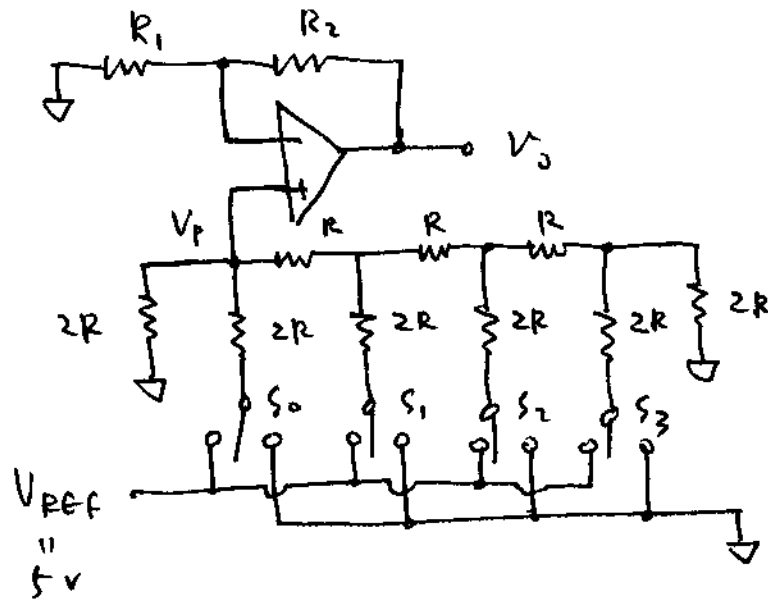

- (i) S_0 ON (V_{REF}) , $V_p = \frac{1}{3} V_{REF}$
- (ii) S_1 ON , $V_p = \frac{1}{2} \times \frac{1}{3} V_{REF}$
- (iii) S_2 ON , $V_p = \frac{1}{2^2} \times \frac{1}{3} V_{REF}$
- (iv) S_3 ON , $V_p = \frac{1}{2^3} \times \frac{1}{3} V_{REF}$

$$V_{FSR} = (1 - 2^{-4}) \times V_{FSR} = 9.375 \text{ V}$$

$$V_p = \left(1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8}\right) \times \frac{1}{3} \times 5 = 3.125 \text{ V}$$

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_p = 9.375 \text{ V}$$

or $R_1 = 1 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$

(b)

8 bit ADC , 0 - 10 V $\frac{10}{255}$

$$V_i = 3.526 \text{ V}$$

비트 : $b_7 b_6 b_5 b_4 b_3 b_2 b_1 b_0$

$$V_i < 5 \text{ V} \Rightarrow b_7 = 0$$

$$V_i > 2.5 \text{ V} \Rightarrow b_6 = 1$$

$$v_i < 3.75 \text{ V} \Rightarrow b_5 = 0$$

$$v_i > 3.125 \text{ V} \Rightarrow b_4 = 1$$

$$v_i > 3.4375 \Rightarrow b_3 = 1$$

$$v_i < 3.59375 \Rightarrow b_2 = 0$$

$$v_i > 3.515625 \Rightarrow b_1 = 0$$

$$v_i < 3.5546875 \Rightarrow b_0 = 0$$

$$\therefore 01011010$$

$$\text{LSB} = \frac{10}{2^8} = 0.0391 \text{ V}$$

$$e_q = \pm \frac{1}{2} \text{ LSB} = \pm 0.0195 \text{ V}$$